

Computer Arithmetic

Chapter Three P&H

Data Representation

- Why do we not encode numbers as strings of ASCII digits inside computers?

Data Representation

- What is **overflow** when applied to binary operations on data?

Data Representation

- Why do we not use signed magnitude to represent numbers inside computers?

Data Representation

- What is the two's compliment number representation?

Data Representation

- How is a two's compliment number sign extended?

Data Representation

- Why does MIPS have:
 - lb and lbu instructions?
 - slt and sltu instructions?

Addition and Subtraction


- No overflow possible when:
 - Adding numbers with different signs
 - Subtracting numbers with same sign
 - one of numbers is zero
- Overflow occurs when:
 - Adding two numbers with same sign and sign of result is different
 - Subtracting numbers with different signs & result is the same sign as second number
- MIPS handles overflow with an exception

MIPS ALU Design

- MIPS ALU requirements
 - add, addu, sub, subu, addi, addiu
 - => 2's complement adder/sub with overflow detection
 - and, or, andi, ori, xor, xori, nor
 - => Logical AND, logical OR, XOR, nor
 - SLTI, SLTIU (set less than)
- => 2's complement adder with inverter, check sign bit of result


Different Implementations

 - Not easy to decide the "best" way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU for addition:




- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?

Building a 32 bit ALU

 


Building a 32 bit ALU

 

What about subtraction (a - b) ?


 
- Two's complement approach: just negate b and add.
- How do we negate?
- A very clever solution:



Tailoring the ALU to the MIPS

- Need to support the set-on-less-than instruction (slt)
 - remember: slt is an arithmetic instruction
 - produces a 1 if $r_s < r_t$ and 0 otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- Need to support test for equality (beq \$t5, \$t6, \$t7)
 - use subtraction: $(a-b) = 0$ implies $a = b$

Supporting slt

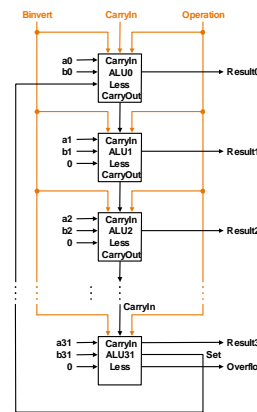 


Test for equality


- Notice control lines:

000 = and
 001 = or
 010 = add
 110 = subtract
 111 = slt

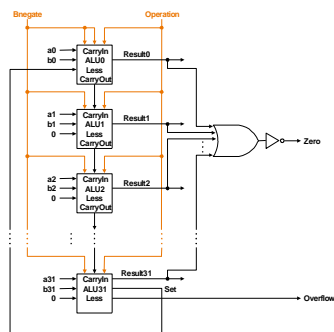*Note: zero is a 1 when the result is zero!




ALU symbol

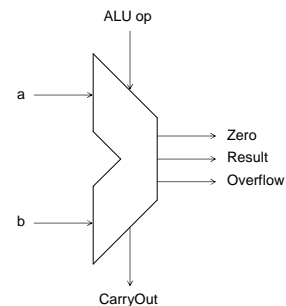

Addition

- Ripple adders are slow

 

- What about sum-of products representation?

$$\begin{aligned} c_1 &= b_0c_0 + a_0c_0 + a_0b_0 & c_2 &= \\ c_2 &= b_1c_1 + a_1c_1 + a_1b_1 & c_3 &= \\ c_3 &= b_2c_2 + a_2c_2 + a_2b_2 & c_4 &= \\ c_4 &= b_3c_3 + a_3c_3 + a_3b_3 & & \end{aligned}$$

Carry Look-ahead Adder

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always generate a carry? $g_i = a_i b_i$
 - When would we propagate the carry? $p_i = a_i + b_i$

$$\begin{aligned} c_1 &= g_0 + p_0c_0 & c_2 &= \\ c_2 &= g_1 + p_1c_1 & c_3 &= \\ c_3 &= g_2 + p_2c_2 & c_4 &= \\ c_4 &= g_3 + p_3c_3 & & \end{aligned}$$

Example

a: 0001 1010 0011 0011
b: 1110 0101 1110 1011

g_i:


p_i:

P₀, P₁, P₂, P₃ ← super propagate.

G₀, G₁, G₂, G₃ ← super generate.

C₄ ← what's that?

Carry Look-ahead Adder

 

Conclusion

- We can build an ALU to support the MIPS instruction set
 - key idea: use multiplexer to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- Important points about hardware
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the "critical path" or the "deepest level of logic")
- Our primary focus: comprehension, however,
 - Clever changes to organization can improve performance (similar to using better algorithms in software)