 


Computer Arithmetic II

Chapter Three P&H

Addition

- Ripple adders are slow



- What about sum-of-products representation?


$$\begin{aligned}
 c_1 &= b_0c_0 + a_0c_0 + a_0b_0 & c_2 &= \\
 c_2 &= b_1c_1 + a_1c_1 + a_1b_1 & c_3 &= \\
 c_3 &= b_2c_2 + a_2c_2 + a_2b_2 & &
 \end{aligned}$$

Carry Look-ahead Adder

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always generate a carry? $g_i = a_i b_i$
 - When would we propagate the carry? $p_i = a_i + b_i$

$$\begin{aligned}
 c_1 &= g_0 + p_0c_0 & c_2 &= \\
 c_2 &= g_1 + p_1c_1 & c_3 &= \\
 c_3 &= g_2 + p_2c_2 & &
 \end{aligned}$$

Carry Look-ahead Adder

 

Example

a: 0001 1010 0011 0011
b: 1110 0101 1110 1011

gi: 0000 0000 0010 0011
pi: 1111 1111 1111 1011

G: 0 0 1 0
P: 1 1 1 0
C: 1 1 1 0

Multiplication

- More complicated than addition
 - accomplished via shifting and addition
- More time and more area
- Let's look at 4 versions based on high school algorithm

$$\begin{array}{r}
 0010 \text{ (multiplicand)} \\
 \times 1011 \text{ (multiplier)} \\
 \hline
 \end{array}$$


Multiplication

```


0010 (2) ← multiplicand
x 1011 (11) ← multiplier
0010
0010
0000
0010
0010
0010110 (22) ← product
    
```

- What logic is required to implement this?
- What can we say about the size requirements to store the product?

Multiplication: 1st Implementation

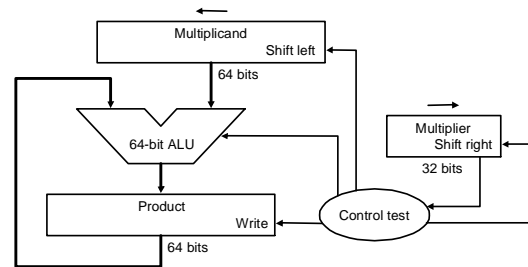

Multiplication: 1st Implementation

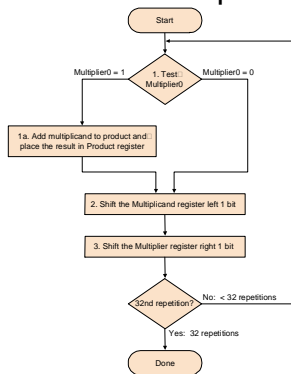


Board Exercise

- $2 \times 3 = 6$
– $0010 \times 0011 = 0110$

Multiplication: 1st implementation performance


- How many steps does this implementation take?
- Is the implementation wasteful in other areas?

Second Version

 

use left hand side of product register.


Second Version

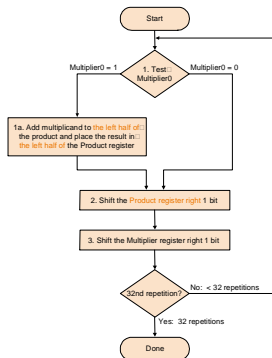

Board Exercise

- $2 \times 3 = 6$
– $0010 \times 0011 = 0110$

Third Version

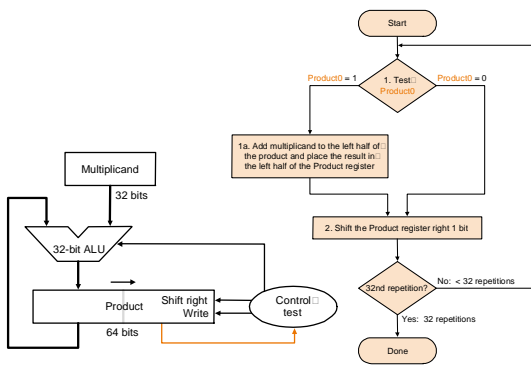

Board Exercise

- $2 \times 3 = 6$
– $0010 \times 0011 = 0110$

Multiplication: Third Implementation performance.

- How many steps does this implementation take?
- What other improvements have been made compared to the first implementation?

Signed multiplication

- An easy (to comprehend) way to do signed multiplication is
 - remember the original signs
 - convert the numbers to positive (temporary working) values
- when is the product negated?
- what extra cycles and resources are required?

Booth's Algorithm

- Does not require conversion cycles
- First step of the third multiplication implementation changes
- Second step (shift product right) remains
- The replacement step depends on the current and previous right-most bits in product
 - 00: no arithmetic op
 - 01: add multiplicand to left half of product
 - 10: sub multiplicand from left half of product
 - 11: no arithmetic op

Board Exercises

- $2 \times -3 = -6$
– $0010 \times 1101 = 1010$

Multiplication by powers of 2

- accomplished using left shift
- e.g. $6 \times 8 = 48$
 - $0110 \times 1000 = 00110000$
 - $6 \times 2^3 = 48$
 - $6 \ll 3 = 48$

Summary

- Multiplication is accomplished by shift and add hardware, using a similar algorithm to that we were taught in school.