


Introduction to VHDL


COMP311

Tony McGregor

G.1.05

tonym@cs.waikato.ac.nz

 


 

What is VHDL?

- **VHSIC Hardware Description Language.**
(VHSIC = Very High Speed Integrated Circuit)
- Allows description of the structure and function of a digital hardware system.
- One of two widely used HDL's.
 - Verilog is the other.
- Both are IEEE standards.
 - VHDL is IEEE Std. 1076 (2002 is the latest)
 - Verilog is IEEE Std. 1364 (2001 is the latest)

Why a Description Language?

 

A description language allows us to create a model of a system

VHDL models can be used to:


- Specify a system so that different people/groups can agree on what the system is.
- Use simulation to test and verify the design
- Formally verify correctness
- Automatic synthesis of circuits

VHDL advantages



- Allows specification of hardware using programming language-like structures.
- Self-documenting design.
- We can ‘synthesise’ a more detailed representation of a design from an abstract one.


Example VHDL

 

```
...


process (reset, clk)
begin
    if reset = '1' then
        counter <= X"0000";
    elsif rising_edge(clk) then
        if up = '1' then
            counter <= counter + X"0001";
        elsif down = '1' then
            counter <= counter - X"0001";
        end if;
    end if;
end process;

...
```

 

Recap – Digital Systems

 - Represented by discrete voltage levels.
- We will deal mostly with binary digital systems.
 - Signals have two possible values
 - ‘1’ or ‘0’
 - TRUE or FALSE
 - ~5V or ~0V
- These systems are built on Boolean algebra.



Boolean Algebra

- Well defined operators for variables which only have two discrete values.


X	NOT X
0	1
1	0

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1


X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0



Transistors

 

 
- Build from silicon
 - a crystal => doesn't transmit electricity
- Can add 'impurities' that create some free electrons (n-type) or 'holes' (p-type)
- The most basic semiconductor is a diode:





Diode

  


NPN Transistor

 


PNP Transistor

  


(Metal Oxide) Field Effect Transistor

 


Gates

 

 
- Using transistors we can implement the Boolean operations in hardware.





CMOS

 

 - reduce power through the use of complementary MOS transistors






NAND Gate

  

A	B	O
0	0	1
0	1	1
1	0	1
1	1	0


NAND VLSI Layout

   

2 Input OR Gate




?

 

input high = on


input low = off

 

input high = off

input low = on

for next year add nand gate diagram

 

Combinational Logic

- output is a function of the current input.
- system has no 'memory' of previous state.


e.g. Consider a two switch hall light

SW1	SW2	Light
off	off	off
off	on	on
on	off	on
on	on	off






Sequential Logic

 - output is a function of the input and the current state.
- circuit must have 'memory' to hold the state.
e.g. consider a lamp that cycles between off, dimly lit, and full brightness with the push of a button.






Basic Storage Elements



- RS latch

   





Enabled SR Flip flop

   





D Latch

  

Falling Edge D Flip flop

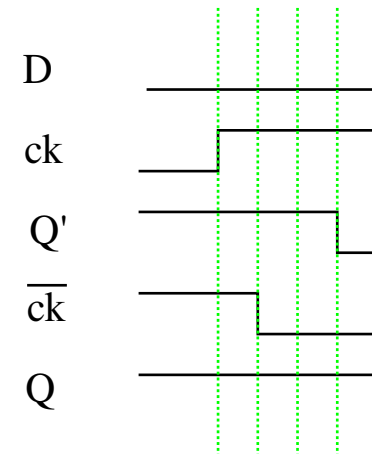   


Rising Edge D Flip Flop

    



A VHDL Entity

 - VHDL designs are divided into units known as ‘entities’.
- an entity consists of a series of signals which may be inputs, outputs or both.




Example entity declaration



```
entity and_gate is  
  port (  
    x : in std_logic;  
    y : in std_logic;  
    output : out std_logic  
  );  
end entity;
```

Architecture

 


```
entity and_gate is  
  port (  
    x : in std_logic;  
    y : in std_logic;  
    output : out std_logic  
  );  
end entity;
```

```
architecture behavioural of and_gate is  
begin  
  output <= x and y;  
end behavioural;
```




Notes about VHDL

 - As with all languages there are often many ways of saying (doing) the same thing.
- VHDL is **case-insensitive**.
- Synthesisable VHDL is a subset of VHDL.
 - Not all VHDL code or structures can be turned into hardware.




Entities

 - The ‘entity’ is a part of the basic design unit in VHDL.
- The entity defines the inputs and outputs of the module, along with ‘generic’ parameters for the implementation.
- We will leave consideration of generics until later.



Entity Declaration Format
 
```
entity entity_name is  
    generic (generic list);  
    port (port definition list);  
end entity_name;
```




Port declaration list

- This specifies the input and output ports for the entity.
- It is a **semicolon-separated** list of:

```
port_name : mode type
```
- **mode** is one of:
 - **in**
 - **out**
 - **inout**
- **type** specifies the datatype.

Example Entity Declaration

 

```
entity and_gate is  
  port (  
    x : in std_logic;  
    y : in std_logic;  
    output : out std_logic  
  );  
end and_gate;
```




Architecture


- Each entity has one or more architectures.
- The architecture defines an implementation of the entity.

Architecture Declaration



```
architecture arch_name of entity_name is  
    ...declarations...  
begin  
    ...concurrent VHDL...  
end arch_name;
```

Example Architecture

 

```
architecture structural of and_gate is  
begin  
    output <= x and y;  
end structural;
```




Libraries

- In VHDL we compile entities, and packages into libraries.
- The working library is generally known as '**work**'.
- The standard VHDL types and operators are in a library known as '**std**'.
- We 'include' a particular library by using this line at the top of our file:

```
library library_name;
```

 - The '**work**' and '**std**' libraries are always available.




Use

- A library may contain various different entities and packages.
- The ‘use’ clause makes part or all of a particular package visible. e.g.

```
use library_name.package_name.item_name;
```


- We can make all of a package visible by using the specifier “**all**”. eg.

```
use ieee.std_logic_1164.all;
```

 

Standard Types

 - VHDL defines a set of standard types and operators.
- These are contained in the 'std' library.
- The types include:
 - bit ('0', '1')
 - boolean (TRUE, FALSE)
 - integer (-??? To +???)
 - natural (0 to integer'high)
 - positive (1 to integer'high)
 - character (ASCII characters e.g. 'D')
 - time (including units e.g. 10us, 15ps...)



The IEEE library


- The IEEE defines a standard library containing several packages with useful functions and types.

- To get to the IEEE library we use:

```
library ieee;
```

- To make one of the IEEE packages visible:

```
use ieee.std_logic_1164.all;
```

 


The std_logic_1164 package

- Provides more powerful types than bit
 - std_ulogic ('U', 'X', '1', '0', 'Z', 'W', 'H', 'L', '-')
 - 0 = forcing 0
 - 1 = forcing 1
 - Z = high impedance
 - L = weak 0 (pull down)
 - H = weak 1 (pull up)
 - U = uninitialised
 - W = weak unknown (strong will override)
 - - = Don't care (no impact on a comparison)
 - X = forcing unknown (will be 1 or 0 but can't tell which)

The std_logic_1164 package



 
- std_logic
 - same as std_ulogic, but `resolved'
 - defined even when two outputs are connected together
- subtypes
 - X01 (subtype of std_ulogic: 'X', '0', '1')
 - X01Z ...
 - UX01 ...
 - UX01Z ...



General notes

- VHDL source files generally have the filename extension `.vhd` or `.vhdl`
- Typically we use one file per entity or package.
- A comment can be placed on a line by preceding it with `--`

Putting it all together...

 

```
library ieee;                -- Use the IEEE library
use ieee.std_logic_1164.all; -- std_logic_1164 package

entity and_gate is
  port (
    x : in std_logic;      -- These are the two input ports
    y : in std_logic;
    output : out std_logic -- This is the output
  );
end and_gate;

architecture structural of and_gate is
begin
  -- Simple concurrent VHDL assignment
  output <= x and y;
end structural;
```