

Introduction to VHDL


-component hierarchy

COMP311


Tony McGregor

G.1.05

tonym@cs.waikato.ac.nz

 


Hierarchy

 

- VHDL is designed to support hierarchical design
 - done by including detailed design into a higher level design
- Build a nand gate from an `and' gate and a `not' gate
- Build a 4-bit (ripple) adder from 4 one bit adders
- Build a CPU from memory, data path, ALU and registers

AND Gate

 


```
library ieee;
use ieee.std_logic_1164.all;
entity and_gate is
    port (
        and_a    : in  std_logic;
        and_b    : in  std_logic;
        and_out   : out std_logic
    );
end and_gate;
architecture rtl of and_gate is
begin
    and_out <= and_a and and_b;
end rtl
```

NOT gate in VHDL




?

NOT gate in VHDL

 

```
library ieee;
use ieee.std_logic_1164.all;
entity not_gate is
    port (
        not_in    : in std_logic;
        not_out   : in std_logic
    );
end not_gate;
architecture structural of not_gate is
begin
    not_out <= not not_in;
end structural
```



NAND gate

 


- build nand from not and and
- build a new entity that references not and and definitions.

```
component and_gate
  port (
    and_a    : in  std_logic;
    and_b    : in  std_logic;
    and_out  : out std_logic
  );
```

NAND VHDL

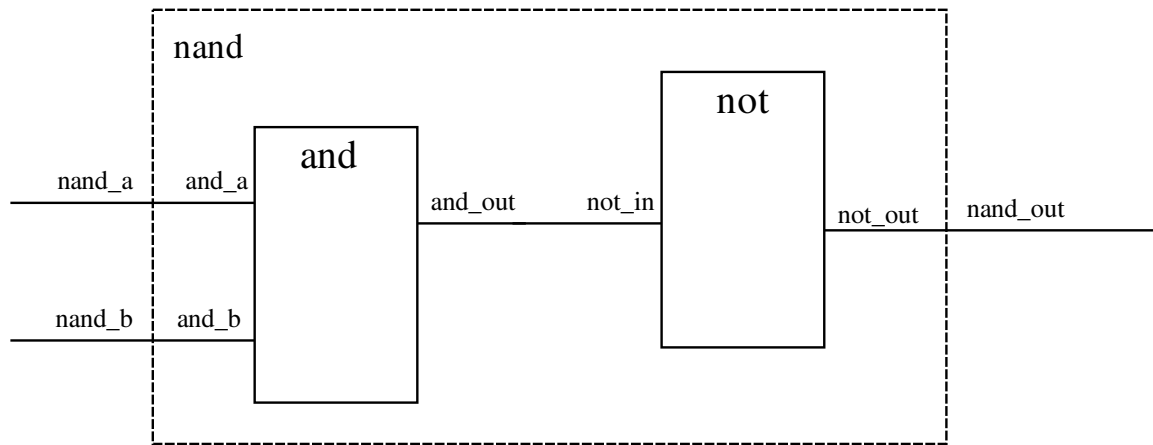 

Nand from and and not

 

```
library ieee;
use ieee.std_logic_1164.all;

entity nand_gate is
  port (
    nand_a   : in  std_logic;
    nand_b   : in  std_logic;
    nand_out : out std_logic
  );
end entity nand_gate;

architecture rtl of nand_gate is
  component and_gate
    port (
      and_a   : in  std_logic;
      and_b   : in  std_logic;
      and_o   : out std_logic);
  end component and_gate;

  component not_gate
    port (
      not_in  : in  std_logic;
      not_out : out std_logic);
  end component not_gate;

  signal and_out_i : std_logic;
```

Begin

```
ANDGATE: and_gate
  port map (
    and_a   => nand_a,
    and_b   => nand_b,
    and_out => and_out_i);
```

```
NOTGATE: not_gate
  port map (
    not_in => and_out_i;
    not_out => nand_out);
```

```
end architecture rtl;
```


Alternative NAND gate syntax



```
library ieee;
use ieee.std_logic_1164.all;

entity nand_gate is
  port (
    nand_a   : in  std_logic;
    nand_b   : in  std_logic;
    nand_out : out std_logic);
end entity nand_gate;


architecture rtl of nand_gate is

  signal and_out_i : std_logic;

begin -- rtl
  ANDGATE: entity and_gate
    port map (
      and_a   => nand_a,
      and_b   => nand_b,
      and_out => and_out_i);

  NOTGATE: entity not_gate
    port map (
      not_in  => and_out_i,
      not_out => nand_out);
end architecture rtl;
```

Revision: 8 bit register in VHDL

 


```
library ieee;
use ieee.std_logic_1164.all;


entity reg_8bit is
  port (
    reset, clk : in std_logic;
    we : in std_logic;
    din : in std_logic_vector(7 downto 0);
    dout : out std_logic_vector(7 downto 0);
  );
end reg_8bit;

architecture rtl of reg_8bit is
begin
  process (reset, clk)
  begin
    if reset = '1' then
      dout <= (others => '0');
    elsif rising_edge(clk) then
      if we = '1' then
        dout <= din;
      end if;
    end if;
  end process;
end rtl;
```

Half Adder

 

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$S \leq A \text{ xor } B$

$C \leq A \text{ and } B$

Half Adder VHDL




```
library ieee;
use ieee.std_logic_1164.all;
entity half is
    port (
        a    : in std_logic;
        b    : in std_logic;
        s    : out std_logic;
        c    : out std_logic
    );
architecture rtl of half is
begin
    s <= a xor b;
    c <= a and b;
end rtl
```

Full Adder




Cin	A	B	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$S \leq (A \text{ xor } B) \text{ xor } \text{Cin}$$
 
$$\text{Cout} \leq ((A \text{ xor } B) \text{ and } \text{Cin}) \text{ or } (A \text{ and } B)$$




Full Adder VHDL

 


```
library ieee;
use ieee.std_logic_1164.all;
entity full is
    port (
        a      : in  std_logic;
        b      : in  std_logic;
        s      : out std_logic;
        cin    : in  std_logic;
        cout   : out std_logic
    );
end full;
architecture rtl of full is
begin
    s    <= (a xor b) xor cin;
    cout <= ((a xor b) and cin) or (a and b);
end rtl
```

4-bit adder

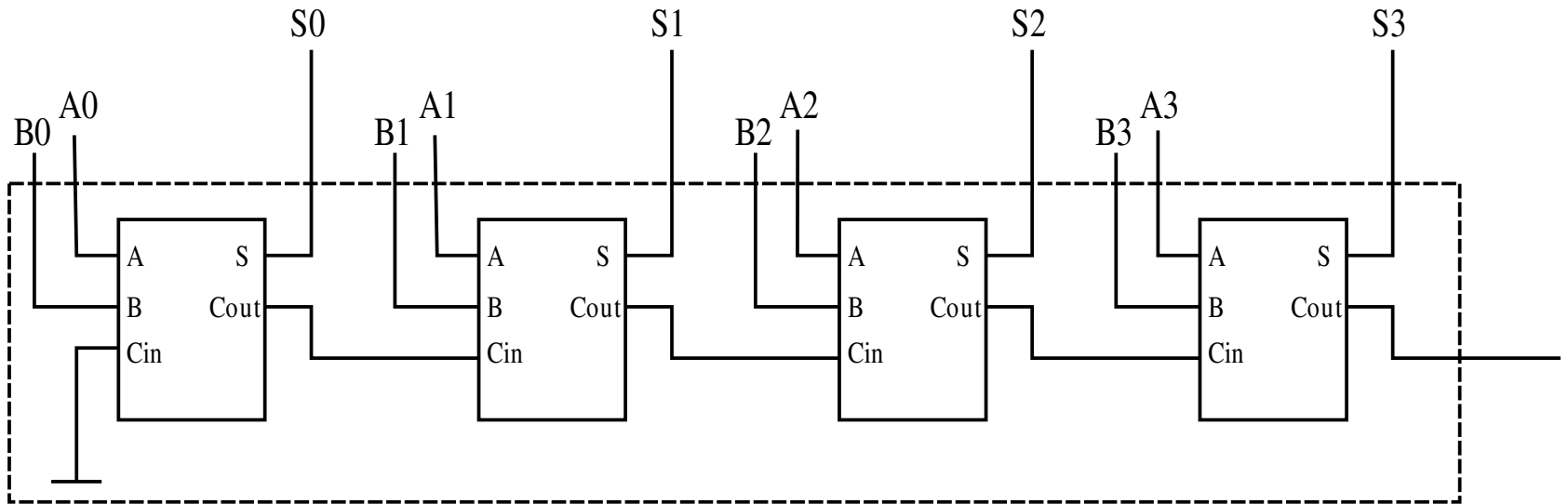

4-bit adder VHDL

 

```
entity add4 is  
  port (  
    a : in  std_logic_vector(3 downto 0);  
    b : in  std_logic_vector(3 downto 0);  
    o : out std_logic_vector(3 downto 0);  
    carry : out std_logic);  
end entity add4;
```


4-bit adder VHDL



```
architecture rtl of add4 is
  signal c : std_logic_vector(2 downto 0);
begin
  bit0: entity full
    port map(a => a(0), b => b(0), s => s(0),
             cin => '0', cout => c(0));

  bit1: entity full
    port map(a => a(1), b => b(1), s => s(1),
             cin => c(0), cout => c(1));

  bit2: entity full
    port map(a => a(2), b => b(2), s => s(2),
             cin => c(1), cout => c(2));

  bit3: entity full
    port map(a => a(3), b => b(3), s => s(3),
             cin => c(2), cout => carry);
end architecture rtl;
```